
 


Sub Circuits used for hierarchical design of the Full adder circuit.

Invertor:


 


```
.option scale=1u

.global Vdd Gnd

.subckt inverter inv_vdd inv_vin inv_vout inv_gnd
M1000 inv_vout inv_vin inv_gnd Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 inv_vout inv_vin inv_vdd inv_vdd pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends
```

Transmission Gate:

  



```
* SPICE3 file created from transgate.ext - technology: scmos


.option scale=1u

.global Vdd Gnd

.subckt transgate trans_clkp trans_vin trans_clkn trans_vout trans_vdd trans_gnd
M1000 trans_vout trans_clkn trans_vin Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 trans_vout trans_clkp trans_vin w_n16_15# pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends
```

Tristate:

  

 

```
* SPICE3 file created from tristate.ext - technology: scmos

.option scale=1u



.global Vdd Gnd

.subckt inverter inv_vdd inv_vin inv_vout inv_gnd
M1000 inv_vout inv_vin inv_gnd Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 inv_vout inv_vin inv_vdd inv_vdd pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt transgate trans_clkp trans_vin trans_clkn trans_vout trans_vdd trans_gnd w_n16_15#
M1000 trans_vout trans_clkn trans_vin Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 trans_vout trans_clkp trans_vin w_n16_15# pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt tristate tri_vin tri_vout tri_clkp tri_clkn tri_vdd tri_gnd
Xinverter_0 tri_vdd tri_vin tri_int tri_gnd inverter
Xtransgate_0 tri_clkp tri_int tri_clkn tri_vout tri_vdd tri_gnd tri_vdd transgate
.ends
```

NAND Gate:

 
 



```
* SPICE3 file created from nand_two.ext - technology: scmos

.option scale=1u

M1000 vdd inB out vdd pfet w=8 l=2
+ ad=112 pd=60 as=80 ps=36
M1001 out inB a_n10_n7# Gnd nfet w=8 l=2
+ ad=56 pd=30 as=80 ps=36
M1002 out inA vdd vdd pfet w=8 l=2
+ ad=0 pd=0 as=0 ps=0
M1003 a_n10_n7# inA gnd Gnd nfet w=8 l=2
+ ad=0 pd=0 as=56 ps=30
```

XOR Gate

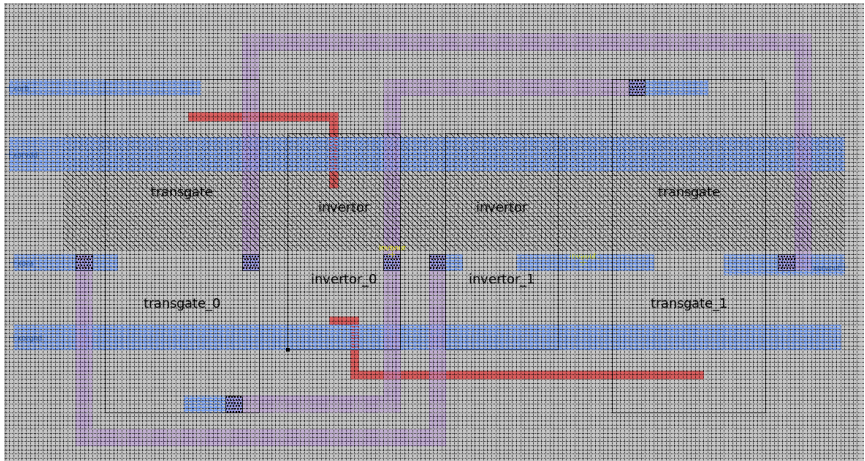 



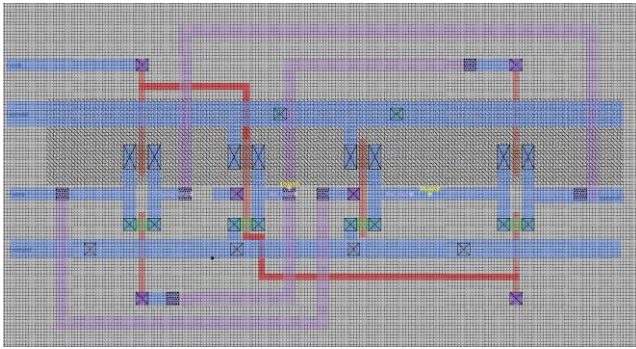


```
.subckt transgate trans_clkp trans_vin trans_clkn trans_vout trans_vdd trans_gnd w_n16_15#
M1000 trans_vout trans_clkn trans_vin Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 trans_vout trans_clkp trans_vin w_n16_15# pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt inverter inv_vdd inv_vin inv_vout inv_gnd
M1000 inv_vout inv_vin inv_gnd Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 inv_vout inv_vin inv_vdd inv_vdd pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt xor xora xorb xorvout xorvdd xorgnd
Xtransgate_1 invbout invaout xorb xorvout xorvdd xorgnd xorvdd transgate
Xinverter_0 xorvdd xorb invbout xorgnd inverter
Xinverter_1 xorvdd xora invaout xorgnd inverter
Xtransgate_0 xorb xora invbout xorvout xorvdd xorgnd xorvdd transgate
.ends
```

OR Gate

   

```
* SPICE3 file created from or.ext - technology: scmos



.option scale=1u


.global Vdd Gnd

.subckt nand_two out inA inB gnd vdd
M1000 vdd inB out vdd pfet w=8 l=2
+ ad=112 pd=60 as=80 ps=36
M1001 out inB a_n10_n7# Gnd nfet w=8 l=2
+ ad=56 pd=30 as=80 ps=36
M1002 out inA vdd vdd pfet w=8 l=2
+ ad=0 pd=0 as=0 ps=0
M1003 a_n10_n7# inA gnd Gnd nfet w=8 l=2
+ ad=0 pd=0 as=56 ps=30
.ends

.subckt or orain orbin orout orvdd orgnd
Xnand_two_0 nand0out orain orain orgnd orvdd nand_two
Xnand_two_1 nand1out orbin orbin orgnd orvdd nand_two
Xnand_two_2 orout nand1out nand0out orgnd orvdd nand_two
.ends
```

AND Gate:

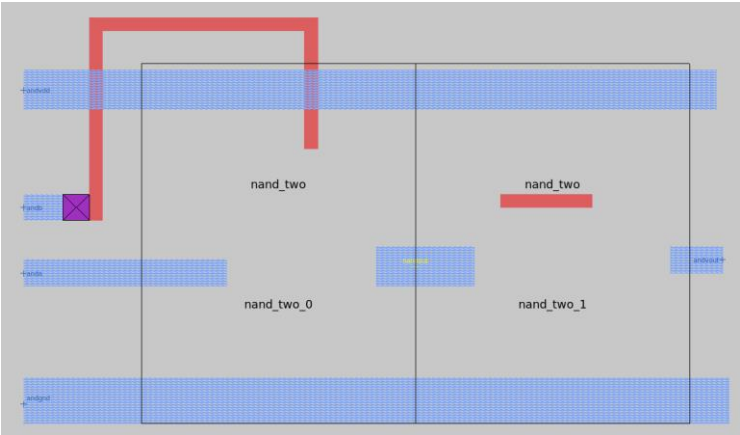 



 


```
.global Vdd Gnd

.subckt nand_two out inA inB gnd vdd
M1000 vdd inB out vdd pfet w=8 l=2
+ ad=112 pd=60 as=80 ps=36
M1001 out inB a_n10_n7# Gnd nfet w=8 l=2
+ ad=56 pd=30 as=80 ps=36
M1002 out inA vdd vdd pfet w=8 l=2
+ ad=0 pd=0 as=0 ps=0
M1003 a_n10_n7# inA gnd Gnd nfet w=8 l=2
+ ad=0 pd=0 as=56 ps=30
.ends

.subckt and anda andb andvout andvdd andgnd
Xnand_two_0 nandout anda andb andgnd andvdd nand_two
Xnand_two_1 andvout nandout nandout andgnd andvdd nand_two
.ends
```

Positive Edge Triggered Flipflop

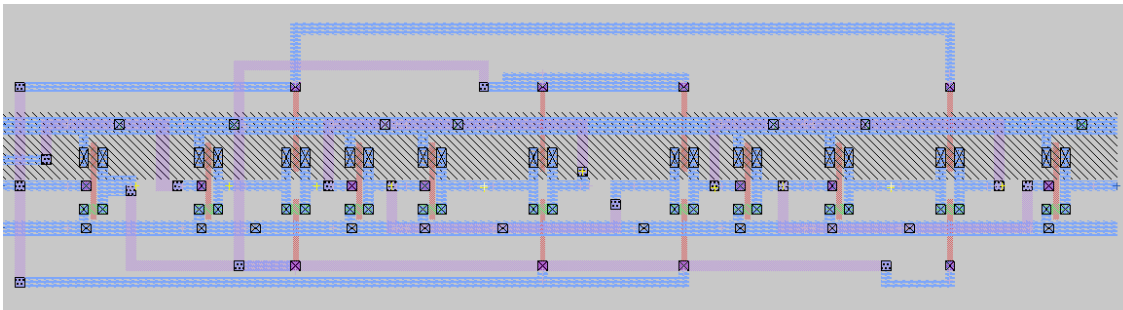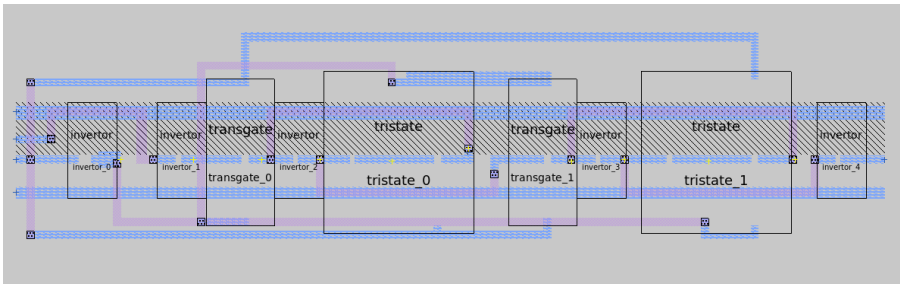 



```
.subckt transgate trans_clkp trans_vin trans_clkn trans_vout trans_vdd trans_gnd w_n16_15#
M1000 trans_vout trans_clkn trans_vin Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 trans_vout trans_clkp trans_vin w_n16_15# pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt inverter inv_vdd inv_vin inv_vout inv_gnd
M1000 inv_vout inv_vin inv_gnd Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 inv_vout inv_vin inv_vdd inv_vdd pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt tristate tri_vin tri_vout tri_clkp tri_clkn tri_vdd tri_gnd tri_int
Xinverter_0 tri_vdd tri_vin tri_int tri_gnd inverter
Xtransgate_0 tri_clkp tri_int tri_clkn tri_vout tri_vdd tri_gnd tri_vdd transgate
.ends

.subckt ff ff_clk ff_din ff_gout ff_vdd ff_gnd
Xtransgate_1 clkp inv2_vout ff_clk try2_vout ff_vdd ff_gnd ff_vdd transgate
Xtristate_0 inv2_vout tryst1_vout clkp ff_clk ff_vdd ff_gnd triint0 tristate
Xtristate_1 inv3_vout try2_vout ff_clk clkp ff_vdd ff_gnd triint1 tristate
Xinverter_0 ff_vdd ff_clk clkp ff_gnd inverter
Xinverter_1 ff_vdd ff_din inv1_vout ff_gnd inverter
Xinverter_2 ff_vdd tryst1_vout inv2_vout ff_gnd inverter
Xinverter_3 ff_vdd try2_vout inv3_vout ff_gnd inverter
Xinverter_4 ff_vdd inv3_vout ff_gout ff_gnd inverter
Xtransgate_0 ff_clk inv1_vout clkp tryst1_vout ff_vdd ff_gnd ff_vdd transgate
.ends
```

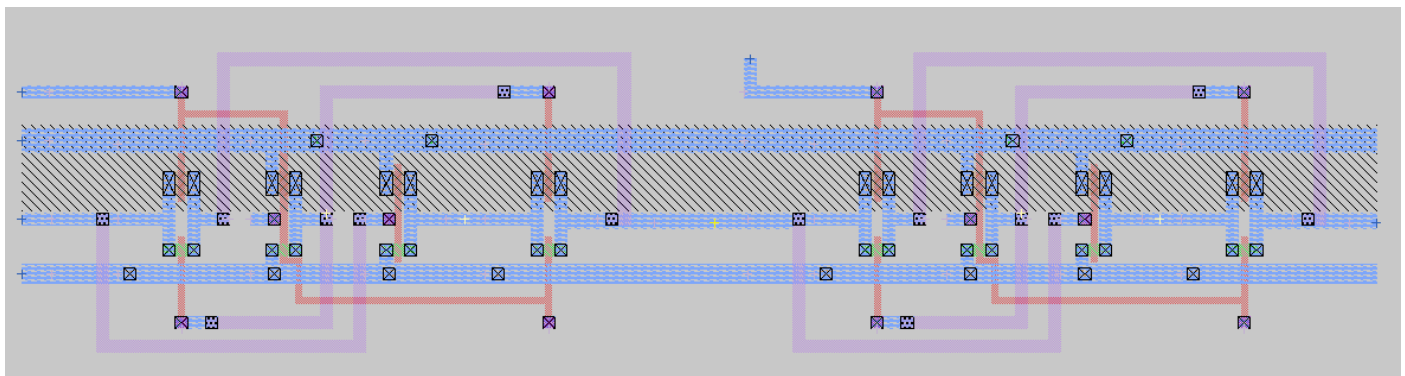 Sum bit of a Full adder = A xor B xor Cin





```
.subckt transgate trans_clkp trans_vin trans_clkn trans_vout trans_vdd trans_gnd w_n16_15#
M1000 trans_vout trans_clkn trans_vin Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 trans_vout trans_clkp trans_vin w_n16_15# pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt inverter inv_vdd inv_vin inv_vout inv_gnd
M1000 inv_vout inv_vin inv_gnd Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 inv_vout inv_vin inv_vdd inv_vdd pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt xor xora xorb xorvout xorvdd xorgnd
Xtransgate_1 inbcout invaout xorb xorvout xorvdd xorgnd xorvdd transgate
Xinverter_0 xorvdd xorb inbcout xorgnd inverter
Xinverter_1 xorvdd xora invaout xorgnd inverter
Xtransgate_0 xorb xora inbcout xorvout xorvdd xorgnd xorvdd transgate
.ends

.subckt sum sumain sumbin sumcin sumvout sumvdd sumgnd
Xxor_0 sumain sumbin xor1out sumvdd sumgnd xor
Xxor_1 xor1out sumcin sumvout sumvdd sumgnd xor
.ends
```

  
Carry bit of Full adder = (B and Cin) or (A and Cin) or (A and B)



```
.subckt nand_two out inA inB gnd vdd
M1000 vdd inB out vdd pfet w=8 l=2
+ ad=112 pd=60 as=80 ps=36
M1001 out inB a_n10_n7# Gnd nfet w=8 l=2
+ ad=56 pd=30 as=80 ps=36
M1002 out inA vdd vdd pfet w=8 l=2
+ ad=0 pd=0 as=0 ps=0
M1003 a_n10_n7# inA gnd Gnd nfet w=8 l=2
+ ad=0 pd=0 as=56 ps=30

.ends

.subckt or orain orbin orout orvdd orgnd
Xnand_two_0 nand0out orain orain orgnd orvdd nand_two
Xnand_two_2 orout nand1out nand0out orgnd orvdd nand_two
Xnand_two_1 nand1out orbin orbin orgnd orvdd nand_two

.ends



.subckt and anda andb andvout andvdd andgnd
Xnand_two_0 nandout anda andb andgnd andvdd nand_two
Xnand_two_1 andvout nandout nandout andgnd andvdd nand_two

.ends

.subckt carry carryain carrybin carrycin carryout carryvdd carrygnd
Xor_0 and1out and0out or0out carryvdd carrygnd or
Xor_1 and2out or0out carryout carryvdd carrygnd or
Xand_0 carryain carrycin and0out carryvdd carrygnd and
Xand_1 carrybin carrycin and1out carryvdd carrygnd and
Xand_2 carrybin carryain and2out carryvdd carrygnd and

.ends
```

  4 bit Ripple Carry Adder: 4 FA Cascaded with carry propagating from previous FA



```
.subckt nand_two out inA inB gnd vdd
M1000 vdd inB out vdd pfet w=8 l=2
+ ad=112 pd=60 as=80 ps=36
M1001 out inB a_n10_n7# Gnd nfet w=8 l=2
+ ad=56 pd=30 as=80 ps=36
M1002 out inA vdd vdd pfet w=8 l=2
+ ad=0 pd=0 as=0 ps=0
M1003 a_n10_n7# inA Gnd Gnd nfet w=8 l=2
+ ad=0 pd=0 as=56 ps=30
.ends

.subckt or orain orbin orout orvdd orgnd
Xnand_two_0 nand0out orain orain orgnd orvdd nand_two
Xnand_two_2 orout nand1out nand0out orgnd orvdd nand_two
Xnand_two_1 nand1out orbin orbin orgnd orvdd nand_two
.ends

.subckt and anda andb andvout andvdd andgnd
Xnand_two_0 nandout anda andb andgnd andvdd nand_two
Xnand_two_1 andvout nandout nandout andgnd andvdd nand_two
.ends

.subckt carry carryain carrybin carrycin carryout carryvdd carrygnd
Xor_0 and1out and0out or0out carryvdd carrygnd or
Xor_1 and2out or0out carryout carryvdd carrygnd or
Xand_0 carryain carrycin and0out carryvdd carrygnd and
Xand_1 carrybin carrycin and1out carryvdd carrygnd and
Xand_2 carrybin carryain and2out carryvdd carrygnd and
.ends
```

```
.subckt transgate trans_clkp trans_vin trans_clkn trans_vout trans_vdd trans_gnd w_n16_15#
M1000 trans_vout trans_clkp trans_vin Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 trans_vout trans_clkp trans_vin w_n16_15# pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt inverter inv_vdd inv_vin inv_vout inv_gnd
M1000 inv_vout inv_vin inv_gnd Gnd nfet w=4 l=2
+ ad=20 pd=18 as=20 ps=18
M1001 inv_vout inv_vin inv_vdd inv_vdd pfet w=8 l=2
+ ad=40 pd=26 as=40 ps=26
.ends

.subckt xor xora xorb xorvout xorvdd xorgnd
Xtransgate_1 invbout invaout xorb xorvout xorvdd xorgnd xorvdd transgate
Xinverter_0 xorvdd xorb invbout xorgnd inverter
Xinverter_1 xorvdd xora invaout xorgnd inverter
Xtransgate_0 xorb xora invbout xorvout xorvdd xorgnd xorvdd transgate
.ends

.subckt sum sumain sumbin sumcin sumvout sumvdd sumgnd
Xxor_0 sumain sumbin xor1out sumvdd sumgnd xor
Xxor_1 xor1out sumcin sumvout sumvdd sumgnd xor
.ends

.subckt fa fa_ain fa_bin fa_cin fa_sout fa_cout fa_vdd fa_gnd
Xcarry_0 fa_ain fa_bin fa_cin fa_cout fa_vdd fa_gnd carry
Xsum_0 fa_bin fa_ain fa_cin fa_sout fa_vdd fa_gnd sum
.ends

.subckt ripple fa_four vdd fa_four_gnd ri_c0 ri_a0 ri_b0 ri_sout0 ri_a1 ri_b1 ri_sout1
+ ri_a2 ri_b2 ri_sout2 ri_a3 ri_b3 ri_sout3 ri_cout
Xfa_0 ri_a0 ri_b0 ri_c0 ri_sout0 ri_c1 fa_four_vdd fa_four_gnd fa
Xfa_1 ri_a1 ri_b1 ri_c1 ri_sout1 ri_c2 fa_four_vdd fa_four_gnd fa
Xfa_2 ri_a2 ri_b2 ri_c2 ri_sout2 ri_c3 fa_four_vdd fa_four_gnd fa
Xfa_3 ri_a3 ri_b3 ri_c3 ri_sout3 ri_cout fa_four_vdd fa_four_gnd fa
.ends
```