

Design Exercise 2


IECE420/520/ICSI522: Introduction to VLSI

Dr. Seetal Potluri

Questions (1 hr)

$$2\lambda = 0.18\mu, L_{\min} = 2\lambda, W_{\min} = 4\lambda$$

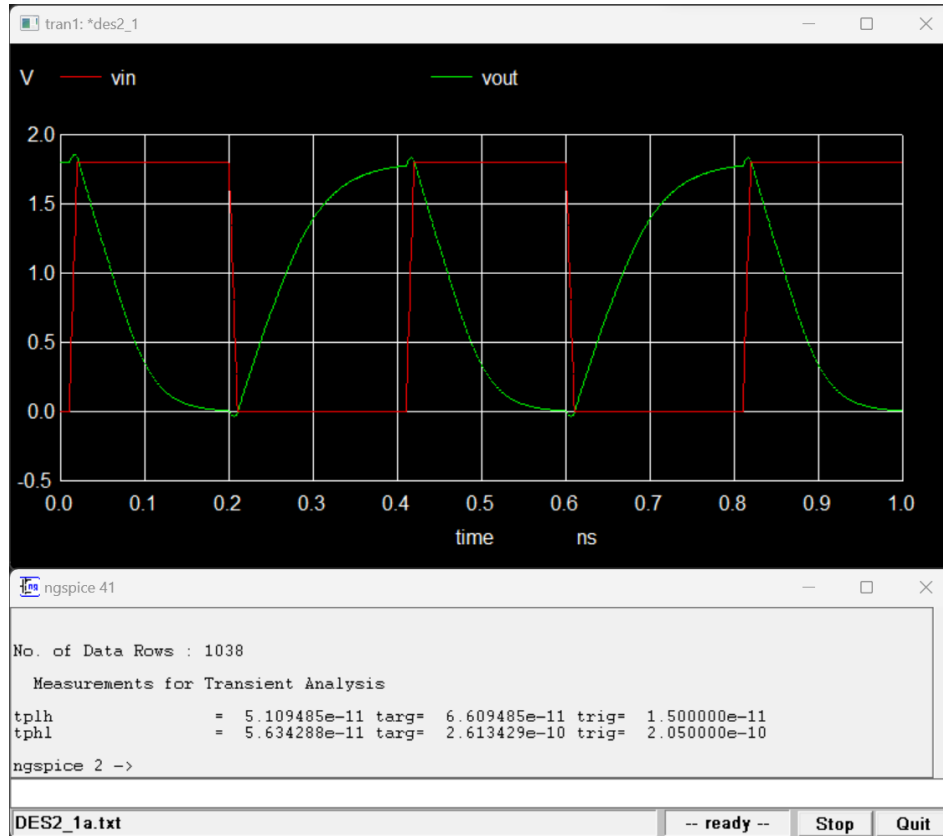1. Let α be the upsizing factor on the unit inverter with a load of 15 fF . Simulate and find α for
- a) $t_{p_{LH}} = t_{p_{HL}} = 50\text{ ps}$ (1 point)



```
*DES2_1
.include bsim.lib

.param alpha = 1.4

VDD vd 0 DC 1.8
VG vin 0 pulse(0 1.8 10p 10p 10p 180p 400p)
Cload vout 0 15F

M1 vout vin 0 0 BSIM3_180nm_N W = '0.36u*alpha' L = 0.18u
M2 vout vin vd vd BSIM3_180nm_P W = '0.72u*alpha' L = 0.18u

.tran 1p 1000p


.measure tran tphl trig v(vin) val=0.9 rise=1 targ v(vout) val=0.9 fall=1
.measure tran tphl trig v(vin) val=0.9 fall=1 targ v(vout) val=0.9 rise=1

.control
run
plot vout vin
.endc

.end
```

$$\alpha = 1.4$$

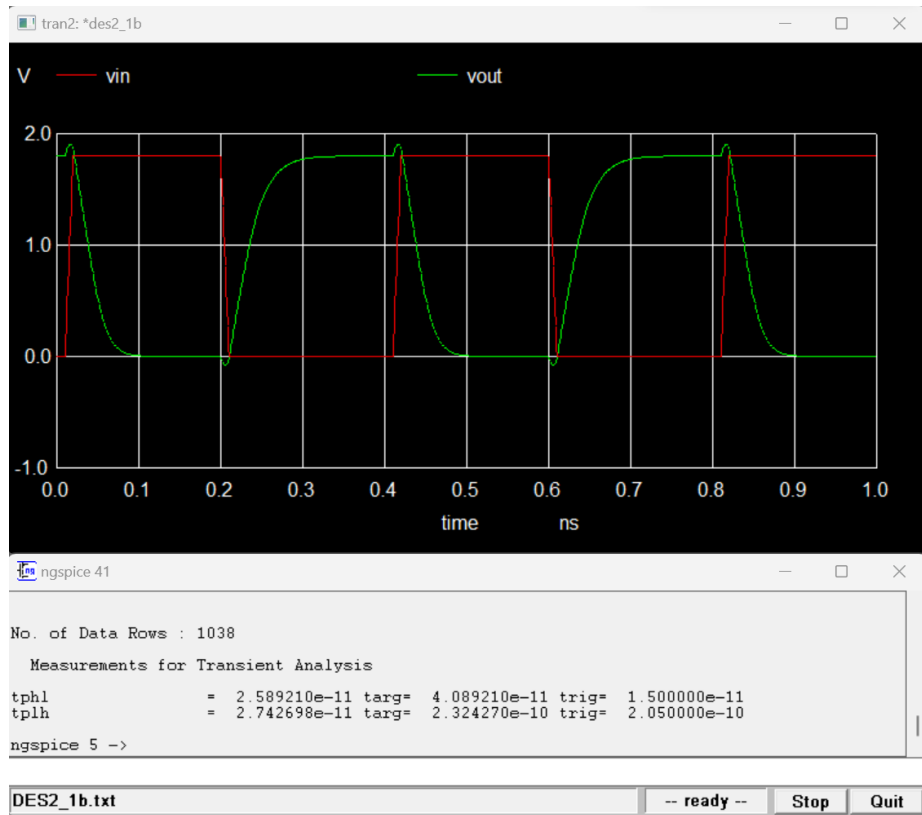b) $tp_{LH} = tp_{HL} = 25 \text{ ps}$ (1 point)



```
*DES2_1b
.include bsim.lib

.param alpha = 4

VDD vd 0 DC 1.8
VG vin 0 pulse(0 1.8 10p 10p 10p 180p 400p)
Cload vout 0 15F

M1 vout vin 0 0 BSIM3_180nm_N W = '0.36u*alpha' L = 0.18u
M2 vout vin vd vd BSIM3_180nm_P W = '0.72u*alpha' L = 0.18u

.tran 1p 1000p

.measure tran tphl trig v(vin) val=0.9 rise=1 targ v(vout) val=0.9 fall=1
.measure tran tplt trig v(vin) val=0.9 fall=1 targ v(vout) val=0.9 rise=1

.control
run
plot vout vin
.endc

.end
```

$\alpha = 4$

2. Simulate and compute static current for a 2-input NAND gate with inputs A and B and with transistor widths chosen to achieve effective fall and rise resistance equal to that of a unit inverter for
- a) $AB = 11$ (1 point)

```
ngspice 41
b          1.8
vout       2.24028e-06
2          1.12014e-06
v2#branch  0
v1#branch  0
vdd#branch -1.18929e-09

No. of Data Rows : 5008
ngspice 6 ->

DES2_2a.txt
```

```
.include bsim.lib

Vdd Vcc 0 dc 1.8
V1 A 0 dc 1.8
V2 B 0 dc 1.8

M1 vout A Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u
M2 vout B Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u

M3 vout A 2 2 BSIM3_180nm_N w=0.72u l=0.18u
M4 2 B 0 0 BSIM3_180nm_N w=0.72u l=0.18u

C1 vout 0 15f

.tran 1p 5000p

.control
Run
Plot A B vout
.endc
.end
```

$$I = 1.18\text{na}$$

b) AB = 01 (1 point)

ngspice 41	
b	0
vout	1.8
2	1.68947
v2#branch	0
v1#branch	0
vdd#branch	-5.51174e-10
No. of Data Rows : 5008	
ngspice 7 ->	
DES2_2b.txt	

$I = 0.551 \text{ nA}$

```
.include bsim.lib

Vdd Vcc 0 dc 1.8
V1 A 0 dc 1.8
V2 B 0 dc 0

M1 vout A Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u
M2 vout B Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u

M3 vout A 2 2 BSIM3_180nm_N w=0.72u l=0.18u
M4 2 B 0 0 BSIM3_180nm_N w=0.72u l=0.18u

C1 vout 0 15f
.tran 1p 5000p
.control
Run
Plot A B vout
.endc
.end
```

c) AB = 00 (1 point)

ngspice 41	
b	0
vout	1.8
2	0.112102
v2#branch	0
v1#branch	0
vdd#branch	-2.45549e-11
No. of Data Rows : 5008	
ngspice 8 ->	

```
.include bsim.lib

Vdd Vcc 0 dc 1.8
V1 A 0 dc 0
V2 B 0 dc 0


M1 vout A Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u
M2 vout B Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u

M3 vout A 2 2 BSIM3_180nm_N w=0.72u l=0.18u
M4 2 B 0 0 BSIM3_180nm_N w=0.72u l=0.18u

C1 vout 0 15f
.tran 1p 5000p
.control
Run
Plot A B vout
.endc
.end
```

$I = 0.024\text{na}$

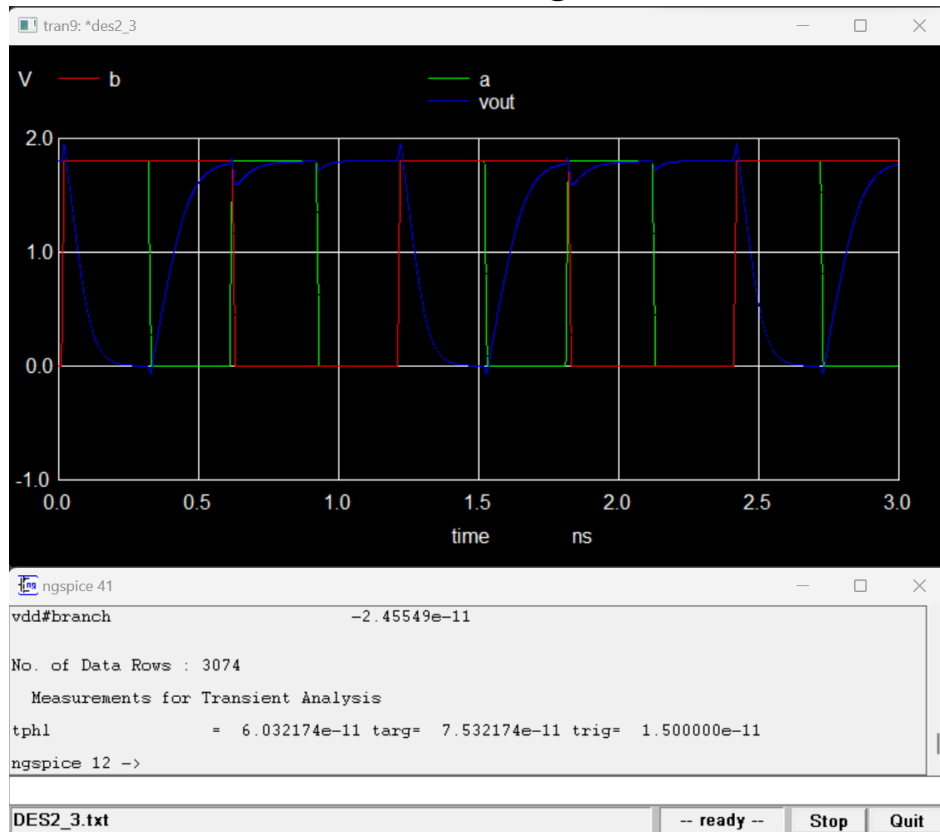3. **5xx**: For the NAND gate above, find tp_{HL} for AB = 00 -> 11 (1 point)



```

.include bsim.lib

Vdd Vcc 0 dc 1.8

VG1 A 0 pulse(0 1.8 10p 10p 10p 300p 600p)
VG2 B 0 pulse(0 1.8 10p 10p 10p 600p 1200p)

M1 vout A Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u
M2 vout B Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u

M3 vout A 2 2 BSIM3_180nm_N w=0.72u l=0.18u
M4 2 B 0 0 BSIM3_180nm_N w=0.72u l=0.18u

.measure tran tphl trig v(A) val=0.9 rise=1 targ v(vout) val=0.9 fall=1


C1 vout 0 15f
.tran 1p 3000p
.control
Run
Plot A B vout
.endc
.end

```

$$tp_{HL} = 60 \text{ psec}$$

4. **5xx extra credit (not for 4xx):** For the NAND gate above, compare t_{pHL} for AB = 00 -> 11 and AB = 01 -> 11(1 point)

Below t_{pHL} for AB = 01 -> 11

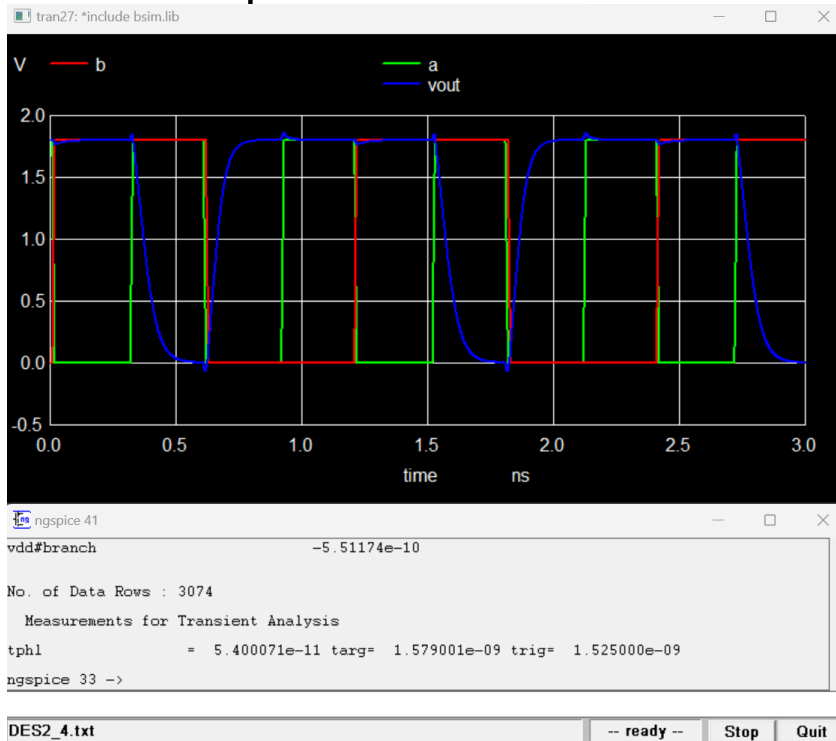

$T_{pHl} = 54$ psec(01 ->11) , $T_{pHl} = 60$ psec(00->11)

Difference is 6psec slower for 00->11 transition

```
.include bsim.lib

Vdd Vcc 0 dc 1.8

VG1 A 0 pulse(1.8 0 10p 10p 10p 300p 600p)
VG2 B 0 pulse(0 1.8 10p 10p 10p 600p 1200p)

M1 vout A Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u
M2 vout B Vcc Vcc BSIM3_180nm_P w=0.72u l=0.18u

M3 vout A 2 2 BSIM3_180nm_N w=0.72u l=0.18u
M4 2 B 0 0 BSIM3_180nm_N w=0.72u l=0.18u

.measure tran tphl trig v(A) val=0.9 rise=3 targ v(vout) val=0.9 fall=2

C1 vout 0 15f
.tran 1p 3000p
.control
Run
Plot A B vout
.endc
.end
```