

Design Exercise 3


IECE420/520/ICSI522: Introduction to VLSI

Dr. Seetal Potluri


Questions

$$2\lambda = 0.18\mu, L_{\min} = 2\lambda, W_{\min} = 4\lambda$$

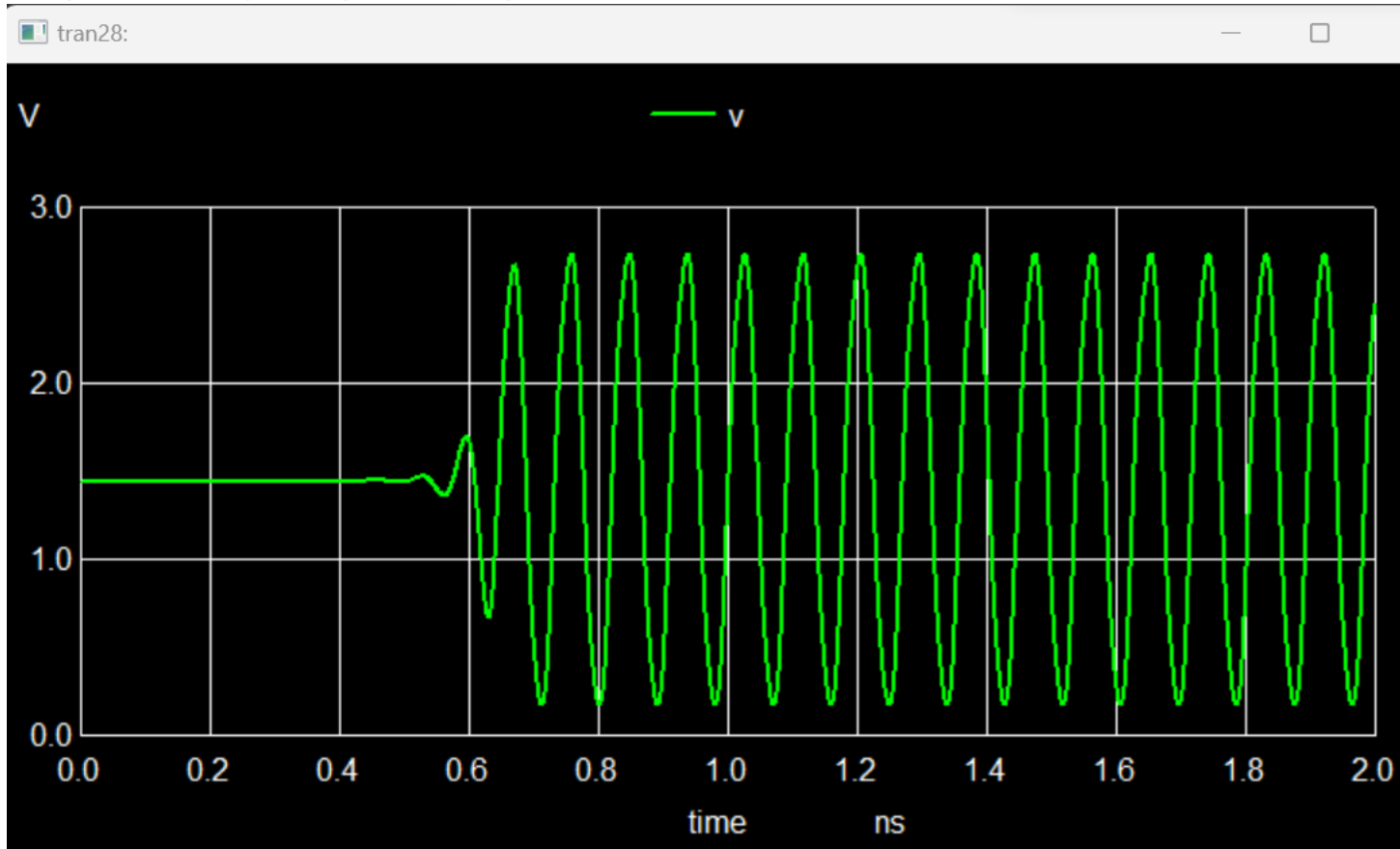
1. Using SPICE, simulate and plot the output for a ring oscillator (built using unit inverters) of
a) 3 stages (1 point)




b) 5 stages (1 point)

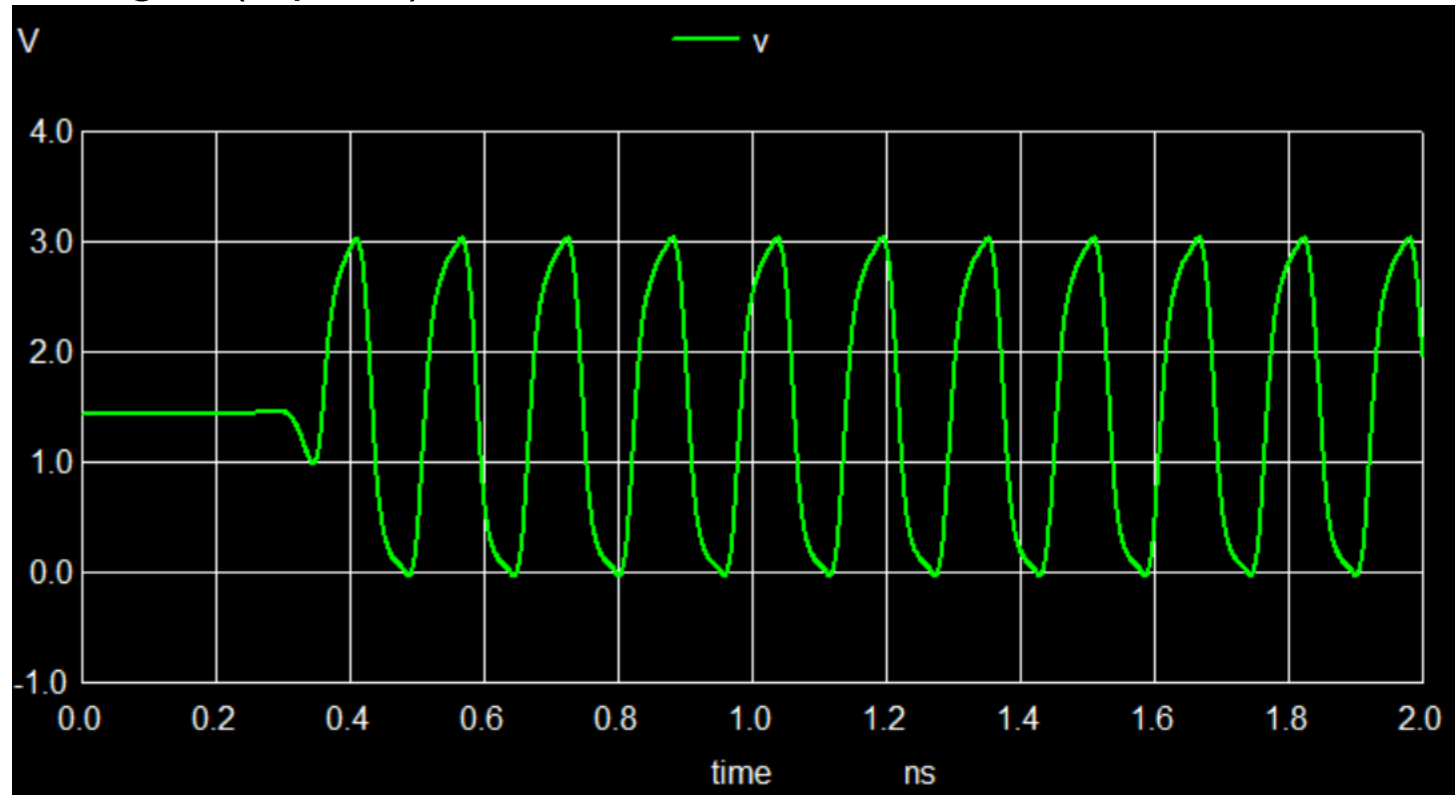

c) 7 stages (1 point)

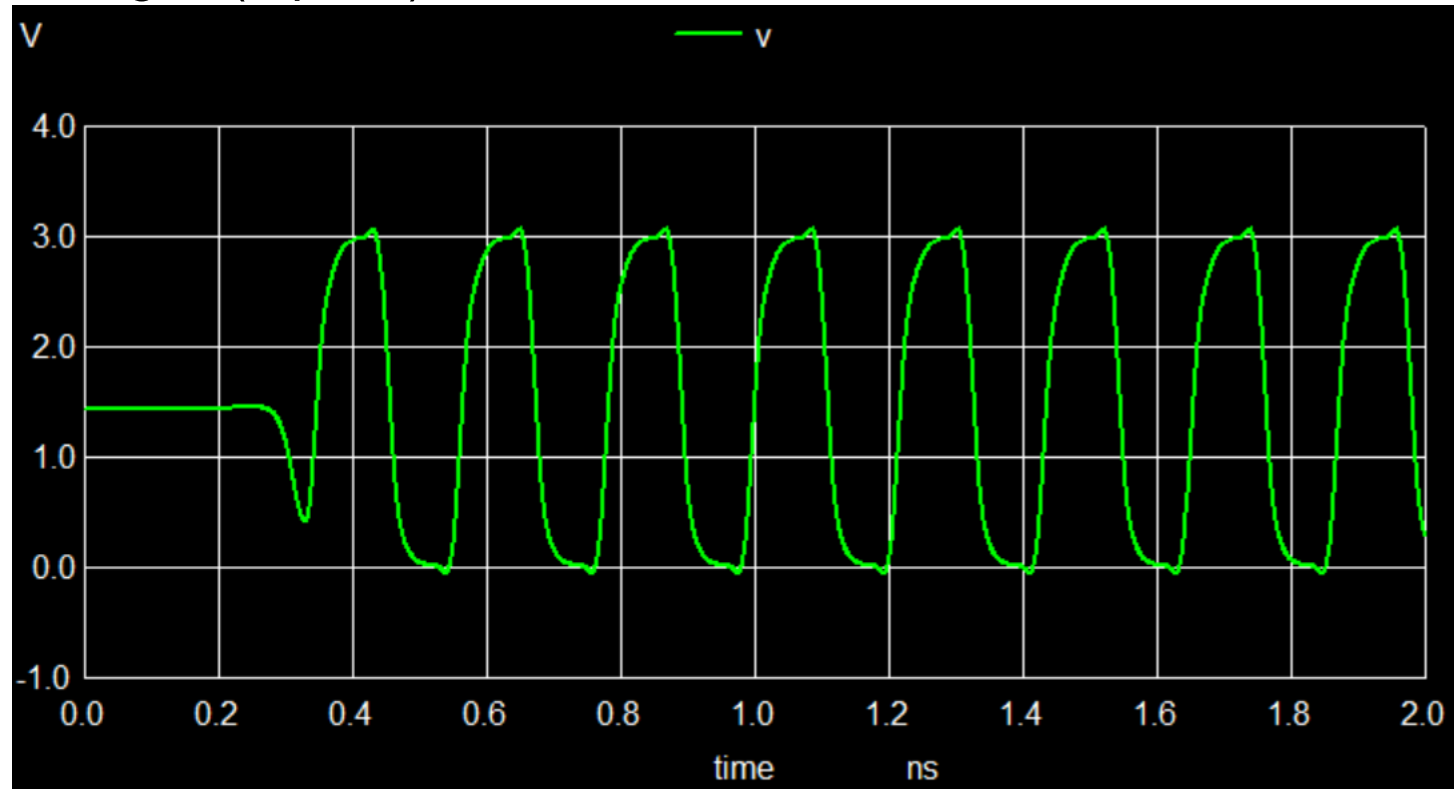


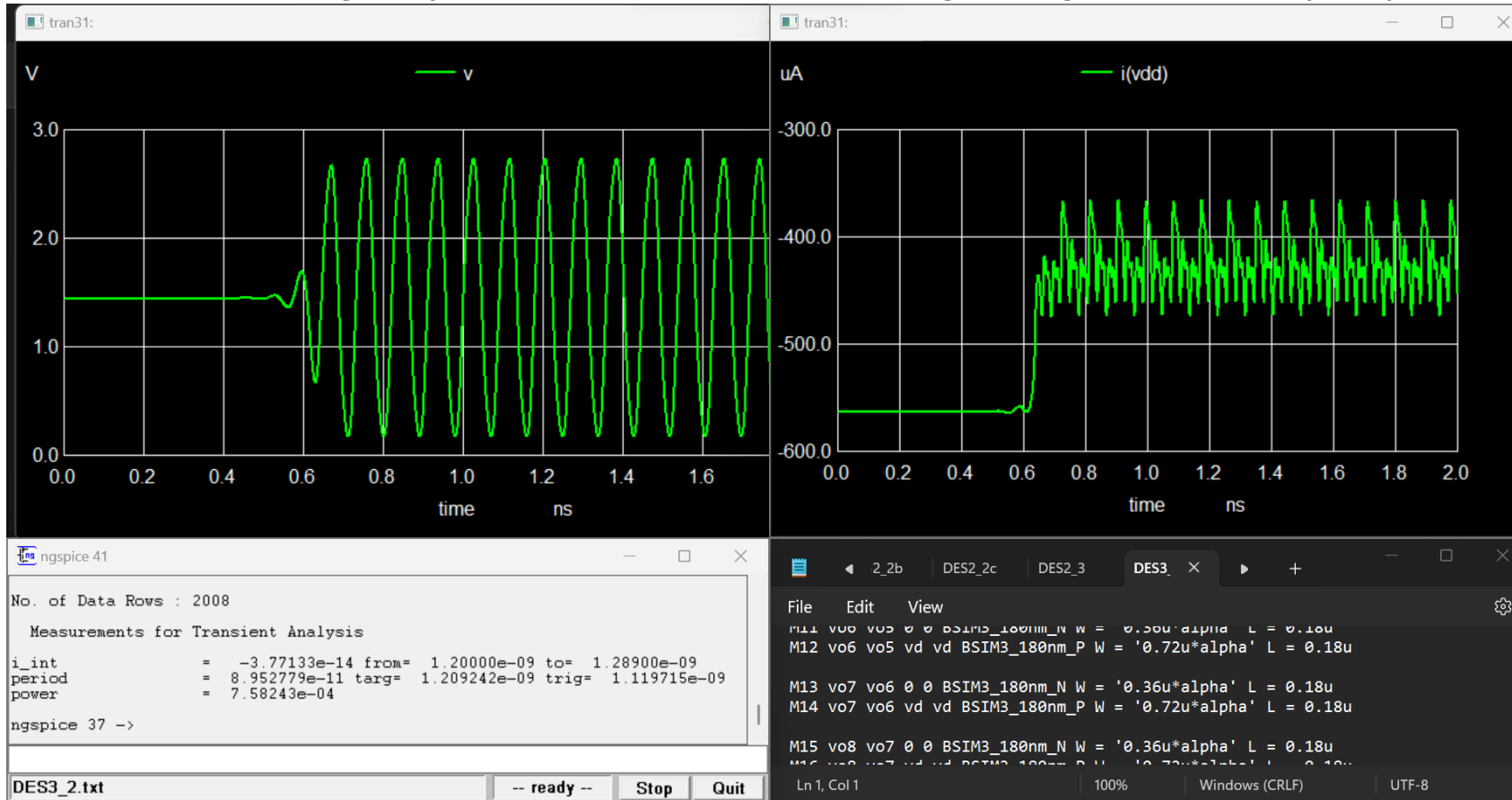2. Compute average dynamic power of a 3-stage ring oscillator (RO) built with unit inverters (2 points)




power = $7.58e-4W$

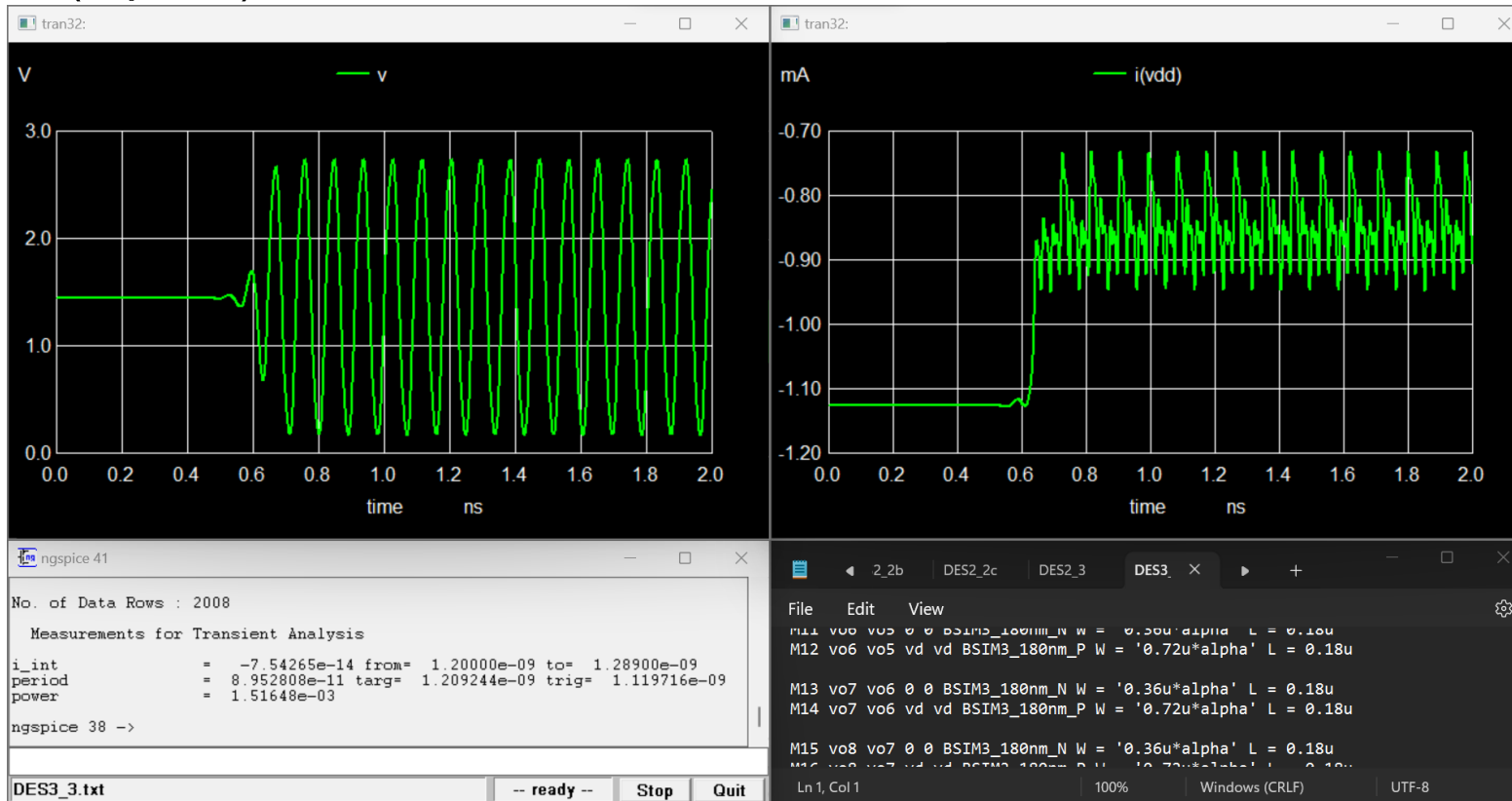3. **5xx (extra credit for 4xx):** Let α be the upsizing factor on the unit inverter. Repeat question 2 with $\alpha = 2$ (1 point)



power = $1.51e-3$ W

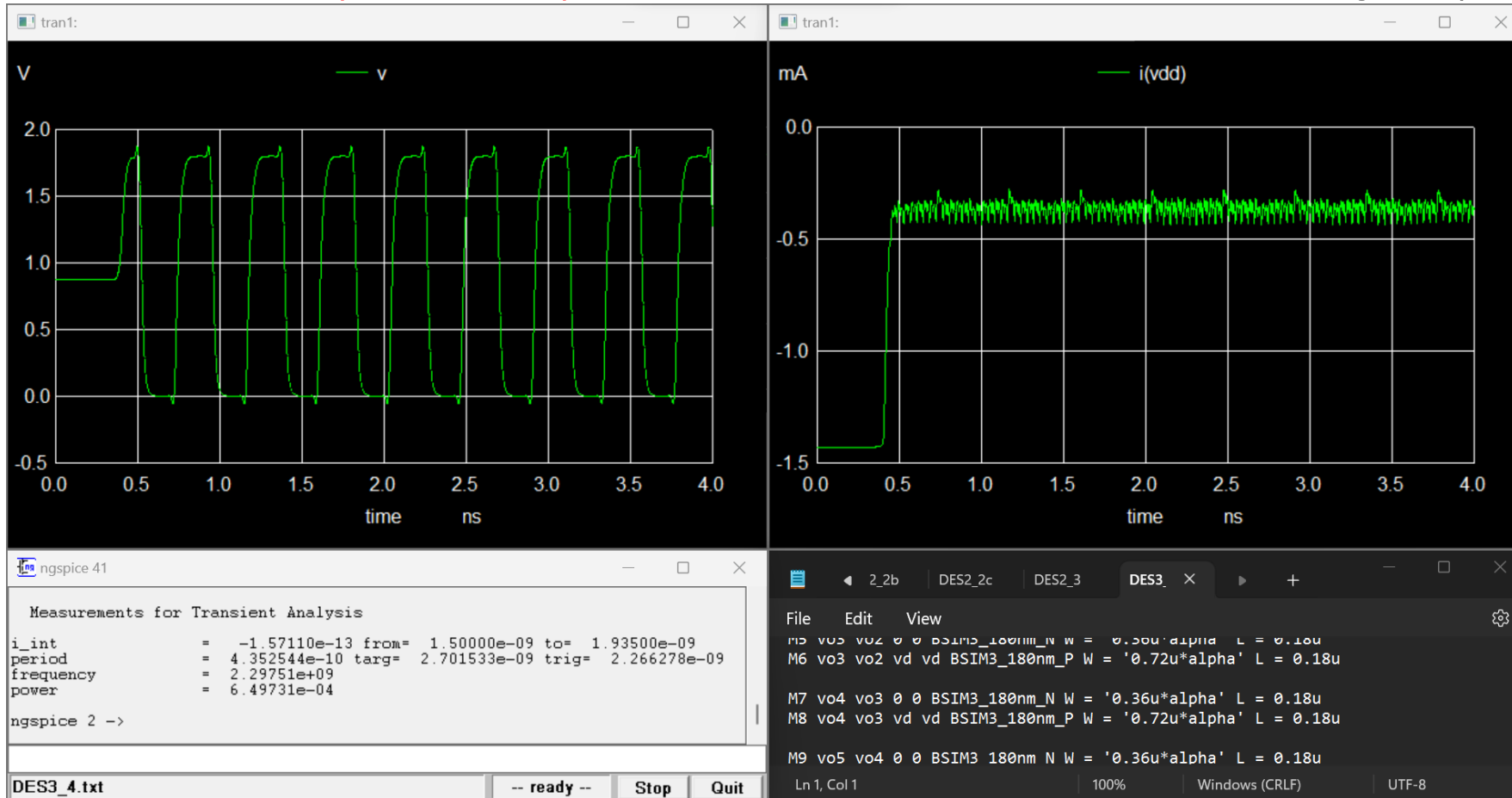4. **5xx extra credit (not for 4xx):** Repeat question 3 for RO with 11 stages (1 point)



Power = $6.49\text{e-}4$ W