

Design Exercise 1


IECE420/520/ICSI522: Introduction to VLSI

Dr. Seetal Potluri

Questions (1 hr 10 min)

$$2\lambda = 0.18\mu, L_{\min} = 2\lambda, W_{\min} = 4\lambda$$

 
1. Simulate the I-V characteristics of a minimum sized NMOS transistor for $V_{GS} = 0 : 0.3V : 1.8V$ (1 pt)



```
*Q1_NMOS
.include bsim.lib
VDD vd 0 DC 1.8
RD vd vout 1k
VG vin 0 DC 1.8
M1 vout vin 0 0 BSIM3_180nm_N W=0.36u L=0.18u


.dc VDD 0 1.8 0.3 VG 0 1.8 0.3
.control
run
plot -VDD#BRANCH
.endc
.end
```

 2. Simulate the I-V characteristics of a minimum sized PMOS transistor for $V_{GS} = 0 : 0.3V : 1.8V$ (1pt)




```
*Q2_PMOS
.include bsim.lib
VDD vd 0 DC -3
RD vd vout 1k
VG vin 0 DC -1.8
M1 vout vin 0 0 BSIM3_180nm_P W=0.36u L=0.18
.dc VDD -3 0 0.1 VG -1.8 0 0.3
.control
run
plot -VDD#BRANCH
.endc
.end
```

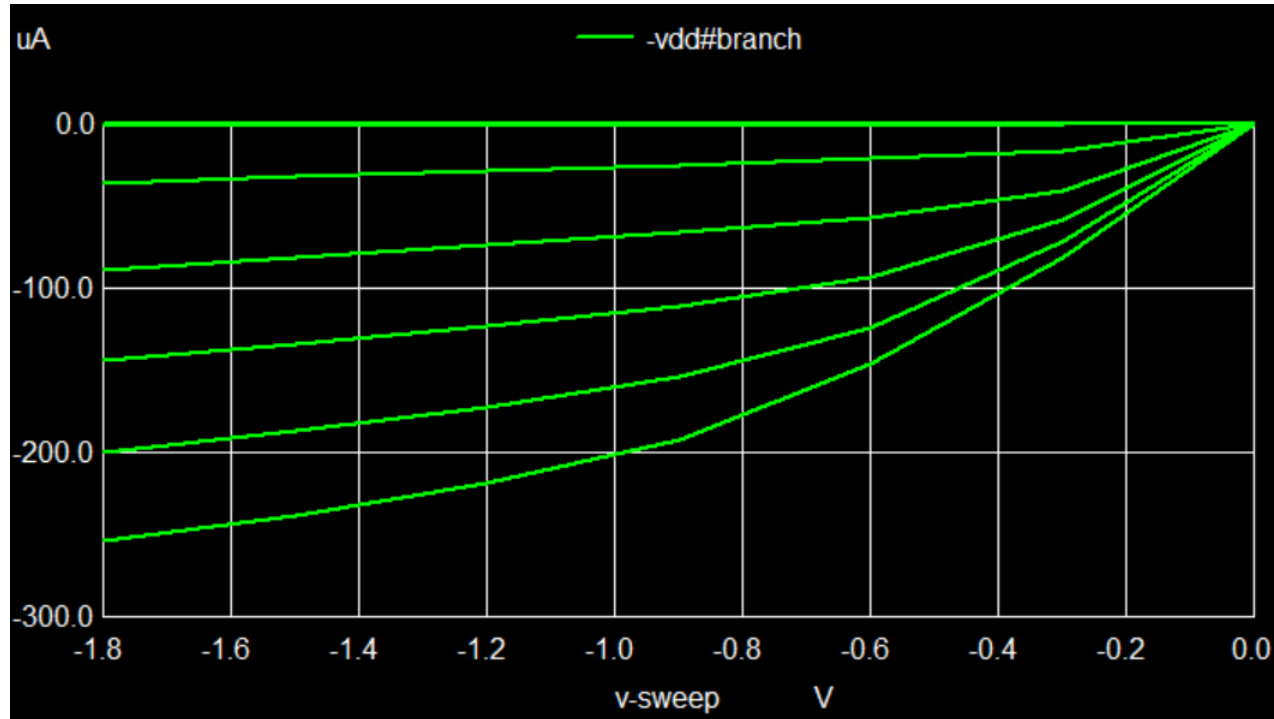3. Size the PMOS so the I-V characteristics match that of minimum sized NMOS (1pt)




```
*Q3_P MOS
.include bsim.lib
VDD vd 0 DC -1.8
RD vd vout 1k
VG vin 0 DC -1.8
M1 vout vin 0 0 BSIM3_180nm_P W=0.8u L=0.18u
.dc VDD -1.8 0 0.3 VG -1.8 0 0.3
.control
run
plot -VDD#BRANCH
.endc
.end
```

 4. Use (3) to simulate the VTC for a symmetric CMOS inverter (2 pt)




```
.include bsim.lib
vdd 3 0 DC 1.8
vin 2 0 DC 0
M1 1 2 3 3 BSIM3_180nm_P W=0.8u L=0.18u
M2 1 2 0 0 BSIM3_180nm_N W=0.36u L=0.18u
.dc vin 0 1.8 0.05
*vdd 0 1.8 0.6
.control
run
plot v(1)
.endc
.end
```

 5. **5xx**: Use minimum size for both NMOS and PMOS and compare VTC with (4) on the same plot (1 pt)



Green is Symmetric CMOS , Red is CMOS using Minimum size. Skewed towards the NMOS for minimum size

 6. **5xx extra credit (not for 4xx):** Use minimum size for NMOS and 4 times the minimum size for PMOS and compare VTC with (4) on the same plot (1 pt)



```
.include bsim.lib
vdd 3 0 DC 1.8
vin 2 0 DC 0
M1 1 2 3 3 BSIM3_180nm_P W=0.36u L=0.18u
M2 1 2 0 0 BSIM3_180nm_N W=0.36u L=0.18u

M3 4 2 3 3 BSIM3_180nm_P W=0.8u L=0.18u
M4 4 2 0 0 BSIM3_180nm_N W=0.36u L=0.18u

M5 5 2 3 3 BSIM3_180nm_P W=1.44u L=0.18u
M6 5 2 0 0 BSIM3_180nm_N W=0.36u L=0.18u

.dc vin 0 1.8 0.05
*vdd 0 1.8 0.6
.control
run
plot v(4) v(1) v(5)
.endc
.end
```

Red is minimum size

Green is symmetric CMOS

Blue is CMOS with PMOS sized six times. (skewed more towards the PMOS)